

Dr. Mahalingam College of Engineering and Technology, Pollachi-3

(An Autonomous Institution affiliated to Anna University)


RETEST (2016 Regulation)


Name of Programme: **B.E - EEE**

Course Code & Course Title: **16EET44 – Networks and Signals**

Sem: IV Date & Session: 06.04.2018 Duration: 1½ hours Max. Marks: 50

Part- A Objective Questions (10X1=10 Marks)

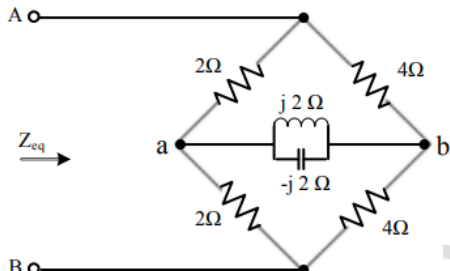Q. No	Question	CO No	Blooms Level
1	If the two ports are connected in cascade configuration, then which arithmetic operation should be performed between the individual transmission parameters in order to determine overall transmission parameters? a) Addition b) Subtraction c) Multiplication d) Division	CO1	R
2	In the circuit shown in figure, the equivalent impedance seen across terminals A, B is 	CO1	U
3	The roots of the odd and even parts of a Hurwitz polynomial P(s) lie on _____ a) right half of s plane b) left half of s-plane c) on jω axis d) on σ axis	CO2	R

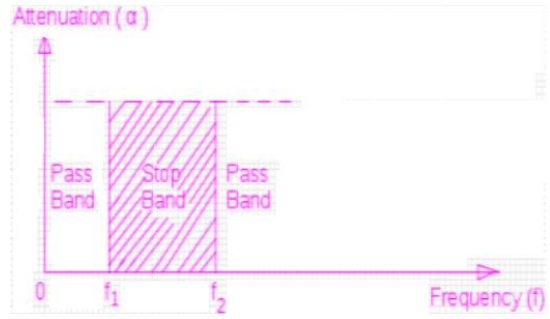4	In the first Foster form, the presence of first element capacitor C_0 indicates _____. a) pole at $\omega=0$ b) pole at $\omega=\alpha$ c) zero at $\omega=0$ d) zero at $\omega=\alpha$	CO2	U
5	The propagation constant of a symmetrical T-section and π – section are the same. Say True/False	CO3	R
6	Identify the type of filter? 	CO3	U
7	Flipping is performed in _____. a) correlation b) convolution c) modulation d) regression	CO4	U
8	Time shifting of discrete time signal means a) $y[n] = x[n-k]$ b) $y[n] = x[-n-k]$ c) $y[n] = -x[n-k]$ d) $y[n] = x[n+k]$	CO4	U
9	An example of a discrete set of information/system is a) the trajectory of the Sun b) data on a CD c) universe time scale d) movement of water through a pipe	CO4	U
10	_____ operation is not associated with the computation process of linear convolution. a) Folding b) Shifting c) Multiplication d) Integration	CO4	U


Part- B Short Answer Questions (5X2=10 Marks)

Q. No	Question	CO No	Blooms Level
11	List the uses of lattice network?	C01	R
12	List the properties of RL Driving point function.	C02	R
13	Check whether $Z(s) = (S+3)/(S+2)$ is a positive real function.	C02	U
14	Find the frequency at which prototype π -section low pass filter having a cut-off frequency f_c has an attenuation of 20dB.	C03	U
15	Find the auto correlation of $x(n)=\{1\ 2\ 1\}$	C04	U

Part- C Descriptive – either or questions (2X15=30 Marks)

Q. No	Question	CO No	Blooms Level
-------	----------	-------	--------------

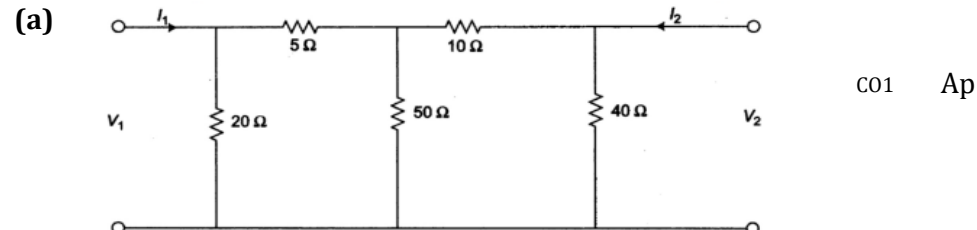16. Find the Y Parameters of the network shown in figure.



OR

16. The driving point impedance of an network is given by

(b)
$$Z(S) = \frac{10S^4 + 12S^2 + 1}{2S(S^2 + 1)}$$
 C02 Ap

Obtain first and second Cauer form.

17. Design an m derived low pass filter(T and π Section) if it has a design resistance of 650 Ω with a cut off frequency of 1500Hz with infinite attenuation frequency of 2000Hz. C03 Ap

OR

17. Find the linear convolution of the following using graphical (b) and tabulation method. $x(n)=\{1\ 2\ 3\ 4\}$; $h(n)=\{1,4,2,1\}$ C04 Ap

Note:

Code for Blooms Levels:

Sl. No.	Blooms Level	Code
1	Remember	R
2	Understand	U
3	Apply	Ap
4	Analyze	An
5	Evaluate	E
6	Create	C

Prepared by (Course Handling Faculty)

Name: M. Sangeetha

Designation: Assistant Professor

Signature with Date

Verified by (Course Coordinator)

Name: Dr.M.Kaliamoorthy

Designation: Assistant Professor

Signature with Date

Approved by:

Head of the Department