

**Dr. Mahalingam College of Engineering and Technology, Pollachi-3**

(An Autonomous Institution)

**CCET I (2016\_Regulation)**


**16EET44 Networks and Signals**


**Answer Key**

Sem:IV Date& Session: **31.01.18(FN1)** Duration: 1½ hours Max. Marks: 50

<b>Part- A Objective Questions (10X1=10 Marks)</b>			
Q. No	Question	CO No	Blooms Level
1	The impedance matrices of two, two port networks are given by $\begin{bmatrix} 3 & 2 \\ 2 & 3 \end{bmatrix}$ and $\begin{bmatrix} 15 & 5 \\ 5 & 25 \end{bmatrix}$ . If the two networks are connected in series. What is the impedance matrix of the combination. a) $\begin{bmatrix} 3 & 5 \\ 2 & 25 \end{bmatrix}$ b) $\begin{bmatrix} 18 & 7 \\ 7 & 28 \end{bmatrix}$ c) $\begin{bmatrix} 3 & 8 \\ 2 & 35 \end{bmatrix}$ d) $\begin{bmatrix} 15 & 2 \\ 5 & 3 \end{bmatrix}$	CO1	U
2	The ABCD parameters of an ideal n:1 transformer is $\begin{bmatrix} n & 0 \\ 0 & x \end{bmatrix}$ . The value of x will be a)x=n b)x=0 c)x=1 d)x=1/n	CO1	AP
3	Which parameters are widely used in transmission line theory a)Z parameters b) Y parameters c)ABCD parameters d)h parameters	CO1	U
4	For a two-port network to be reciprocal. a) $Z_{11}=Z_{22}$ b) $h_{21}=-h_{12}$ c) $Y_{21}=Y_{22}$ d)AD-BC=0	CO1	U


5	For a lattice network the value of the series impedance is $3\Omega$ and that of the diagonal impedance is $5\Omega$ , then Z parameters of the network are given by a) $Z_{11}=Z_{22}=2\Omega$ , $Z_{12}=Z_{21}=1/2\Omega$ , b) $Z_{11}=Z_{22}=4\Omega$ , $Z_{12}=Z_{21}=1\Omega$ , c) $Z_{11}=Z_{22}=8\Omega$ , $Z_{12}=Z_{21}=2\Omega$ , d) $Z_{11}=Z_{22}=5\Omega$ , $Z_{12}=Z_{21}=2\Omega$ ,	CO1	U
6	The expression of A in transmission parameter interms of Z parameter $A=Z_{11}/Z_{21}$	CO1	U
7	In the first Foster form the presence of last element inductor $L\propto$ indicates (a) pole at $\omega=0$ (b) pole at $\omega = \infty$ (c) zero at $\omega = \infty$ (d) zero at $\omega=0$	CO1	U
8	An LC impedance or admittance function _____ (a) has simple poles and zeros in the left half of the s-plane. (b) has no zero or pole at the origin or infinity. (c) is an odd rational function. (d) has all poles on the negative real axis of the s-plane	CO2	U
9	Poles and Zeros are called critical frequencies. <b>True</b>	CO2	U
10	Pole at infinity indicates that the a)degree of numerator is greater than that of denominator b) degree of denominator is greater than that of numerator c) degree of denominator is equal to degree of numerator	CO2	U

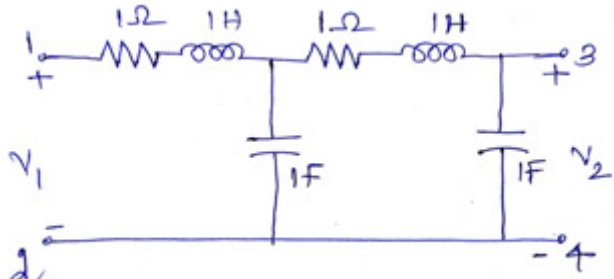Part- B Short Answer Questions (5X2=10 Marks)			
Q. No	Question	CO No	Blooms Level
11	<p><b>(i) Driving point impedance</b> The ratio of transform voltage at one port to the transform current at the same port. <math>Z_{11}(s)=V_1(s)/I_1(s)</math></p> <p><b>(ii) Transfer impedance</b> The ratio of transform voltage at one port to the transform current at the other port. <math>G_{21}(s)=V_2(s)/I_1(s)</math></p>	CO1	U
12	<p>For the ladder two-port network shown find the open circuit driving point impedance at port 1-2</p>  <p>Ans:</p> $Z_{11} = \frac{s^4 + 2s^3 + 3s^2 + 3s + 2}{s^3 + s^2 + s + 1}$	CO1	U
13	<p>Draw the pole zero plot for a given network function.</p> $Z(s) = \frac{3s(s+1)^2(s+5)}{(s+1)(s+3+j2)(s+3-j2)}$	CO1	U

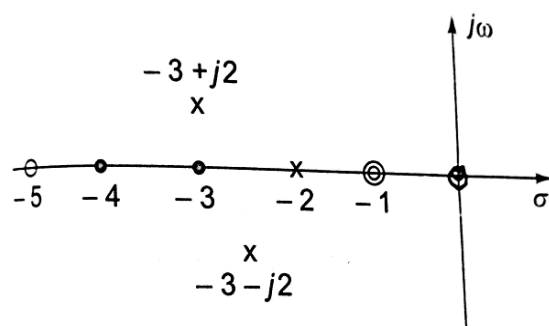			
14	<p>List out the properties of RL impedance function</p> <ul style="list-style-type: none"> <li>• Poles and zeros are located on the negative real axis of s-plane</li> <li>• Poles and Zeros are interlaced</li> <li>• <math>S=0</math> at zero &amp; <math>S=\infty</math> at pole</li> <li>• The residues at the poles are real and negative</li> </ul>	CO2	U
15	<p>suitable network for the following impedance function.</p> <p>(i) <math>Z(s) = \frac{(s+1)(s+4)(s+3)}{s(s+2)(s+6)}</math></p> <p><b>Ans: RC network</b></p> <p>(ii) <math>Z(s) = \frac{s(s^2 + 4)}{(s^2 + 1)(s^2 + 25)}</math> <b>Ans: LC network</b></p>	CO2	U

**Part- C Descriptive – either or questions (2X15=30 Marks)**

Q. No	Question	CO No	Blooms Level
16. (a)	Find the transmission or general circuit parameters of the given network	CO1	

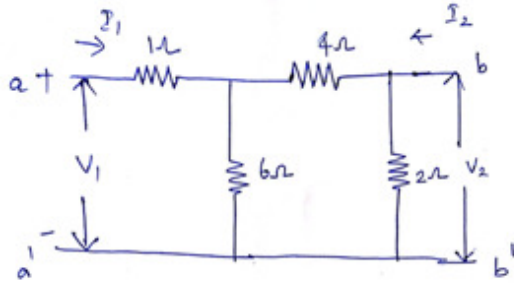

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

$$V_1 = 4I_1$$

$$V_2 = 2 \times \text{flow at } 2 \Omega$$

$$I_{2A} = I_1 \times \frac{6}{12} = \frac{I_1}{2}$$

$$V_2 = 2 \times \frac{I_1}{2} \Rightarrow V_2 = I_1$$

$$A = \frac{4I_1}{I_1} \Rightarrow A = 4$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{I_1}{I_1}$$

$$C = 1$$

$$B = - \left. \frac{V_1}{I_2} \right|_{V_2=0}$$

$$V_1 = 3.4 I_1$$

$$I_2 = -I_1 \times \frac{6}{10} = -0.6 I_1$$


$$B = \frac{3.4 I_1}{0.6 I_1} \Rightarrow B = 5.66$$

$$D = - \left. \frac{I_1}{I_2} \right|_{V_2=0} = \frac{-I_1}{-0.6 I_1}$$

$$D = 1.66$$

**OR**

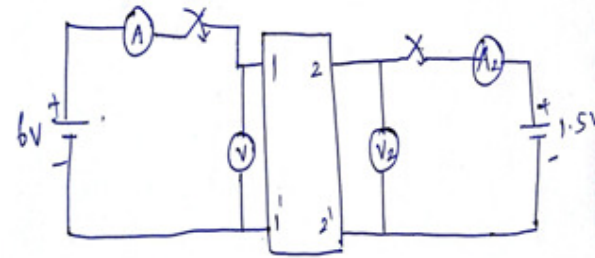16. (i)  $S_1$  - open  $S_2$  - closed  $A_1=0A$   $V_1=4.5V$   $V_2=1.5V$   $A_2=1A$   
 (ii)  $S_1$  - open  $S_2$  - open  $A_1=4A$   $V_1=6V$   $V_2=6V$   $A_2=0A$



$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = \frac{4.5}{1.5} = 3$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{1}{1.5} = 0.67$$

$$Z = \begin{bmatrix} 1.5 & 4.5 \\ 1.5 & 1.5 \end{bmatrix}$$

$$h = \begin{bmatrix} -3 & 3 \\ -1 & 0.67 \end{bmatrix}$$

CO1 **Ap**

17. (a) Analyse in Foster I and Foster II forms of realization of

CO2 **An**

following driving point function  $Z(s) = \frac{2s^2 + 12s + 16}{s^2 + 4s + 3}$

Foster - I


Ans:  $Z(s) = 2 + \frac{3}{s+1} + \frac{1}{s+2}$

$$Z(s) = \frac{P_0}{s} + \frac{P_n}{s+\sigma_n} + \dots + H$$

$$H \rightarrow R_0 \quad P_0 = \frac{1}{C_0} \quad \sigma_n = \frac{1}{R_n C_n}$$

$$R_1 = 2\Omega, R_2 = \frac{1}{3}\Omega, R_0 = 2\Omega$$

$$C_1 = \frac{1}{3}F \quad C_2 = 1F$$

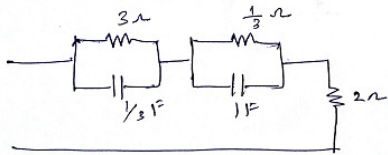

Foster - II


Ans:  $Y(s) = \frac{3}{16} + \frac{\frac{3}{16}s}{s+4} + \frac{\frac{1}{4}s}{s+2}$

$$Y(s) = P_0 + \frac{P_1 s}{s+\sigma_1} + \dots + H$$

$$P_0 = \frac{1}{R_0} \quad \sigma_n = \frac{1}{C_n R_n}$$

$$R_0 = \frac{16}{3}, R_1 = \frac{16}{3}, R_2 = 8$$
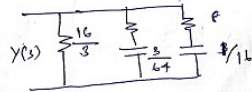
$$C_1 = \frac{3}{64}, C_2 = \frac{1}{16}$$




OR


17. Ans:

(b)

Cauer - I

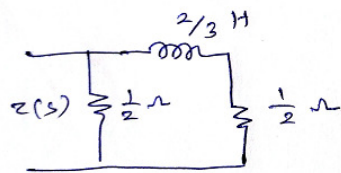

Cauer - II

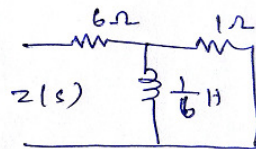

C02

An