

**Dr. Mahalingam College of Engineering and Technology, Pollachi-3**

(An Autonomous Institution)

**CCET II (2016Regulation)**Name of Programme: **B.E - EEE**Course Code & Course Title: **16EET44 - Networks and Signals**

Sem:IV Date &amp; Session:16.03.2018 (FN1) Duration: 1½ hours Max. Marks: 50

**Part- A Objective Questions (10X1=10 Marks)**

Q. No	Question	CO No	Blooms Level
1	An ideal filter should have ____ a) zero attenuation in the pass band b) infinite attenuation in the pass band c) zero attenuation in the attenuation band d) infinite attenuation in the cutoff point	C03	U
2	The values of L and C for a low pass filter with cutoff frequency of 2.5 KHz to operate with a terminated load resistance of 450 ohms are given by ____ a) 57.32 mH; 0.283 µF b) 28.66 mH; 0.14 µF c) 114.64 mH; 0.566 µF d) 85.98 mH; 0.42 µF	C03	R
3	A band pass filter is obtained by using a high pass filter followed by low pass filter. Say True or False	C03	R
4	The attenuation is not sharp in the stop band for ____ filters.	C03	R
5	In m derived low pass filters , the resonant frequency is to be chosen so that it is a) Above cut off frequency	C03	U

b) Below the cutoff frequency

c) Equal to cut off frequency

d) half of the cut off frequency

6	An LTI system is said to be linear if and only if it satisfies the principle of ____	C04	U
7	The integral of impulse function gives a) Step function b) Ramp function c) Pulse function d) Exponential function	C04	R
8	Non deterministic signals are also called as ____ a) Thermal noise b) Ramp signals c) Random signals d) Sinusoidal signals	C04	R
9	A signal is said to be energy signal if ____	C04	U
10	Digital impulse signal is defined by the sequence a) $\delta(n) = 1, n=0$ 0, $n < 0$ b) $\delta(n) = 1, n=0$ 0, $n \neq 0$ c) $\delta(n) = 1, n=0$ 0, $n > 0$ d) $\delta(n) = 1, n < 0$ 0, $n \neq 0$	C04	U

**Part- B Short Answer Questions (5X2=10 Marks)**

Q. No	Question	CO No	Blooms Level
11	Draw the symmetrical T and $\pi$ representation of filter network.	C03	R
12	Design a high pass T-section filter having a cut-off frequency of 1000Hz to operate with a terminated load resistance of 600Ω.	C03	U
13	Differentiate pass band and stop band filters.	C03	R

**14** Distinguish between Energy and Power signals.

CO4 U

**15** List the classifications of signals.

CO4 R

iii) If  $x(n) = \{0, 2, -1, 0, 2, 1, 1, 0, -1\}$  determine  $x(n-3)$  and  $x(-n)$ . Also represent graphically. (4)

**Note: Code for Blooms Levels:**

**Part- C Descriptive – either or questions (2X15=30 Marks)**

Q. No	Question	CO No	Blooms Level
-------	----------	-------	--------------

**16.** (i) Derive the characteristic impedance of constant K low pass filter and also draw the impedance curve with frequency. (10)

CO3 U

(ii) Design a low pass filter (T or pi network) having the cut off frequency of 2 kHz with load resistance of  $500\Omega$ . (5)

**OR**

**16.** Design a m derived high pass filter with a cut off frequency of 10KHz, design impedance of  $5\Omega$  and  $m=0.4$ .

CO3 U

**17.** Check the following systems are causal or non-causal, time variant or invariant, linear or nonlinear, static or dynamic, stable or unstable.

CO4 Ap

(i)  $y(n) = x(2n)$  (ii)  $y(n) = Ax(n) + B$  (7) (iii)  $y(n) = n x(n)$

**OR**

**17.** i) Check whether the following signals are periodic and find its fundamental period. (6)

$x(n) = \sin 2\pi n$  and  $x(n) = \cos 2\pi n + \cos 8\pi n$

CO4 Ap

ii) Check the signal  $x(n) = \sin(n\pi/3)$  is energy signal or power signal. (5)

Sl. No.	Blooms Level	Code
1	Remember	R
2	Understand	U
3	Apply	Ap
4	Analyze	An
5	Evaluate	E
6	Create	C